

COMP311-1: Logic Circuit Design

Fall 2019, Prof. Taigon Song

Project 2. Due: Dec. 2, 8:59am [Total: 90 + 10 points]

2015112138


Se Jin Kwon

No.	Checksheet item	Done?[Y/N]
1	RCA adder design (no delay, 10 points)	Y
2	CLA adder design (no delay, 20 points)	Y
3	CSA adder design 1 (no delay, 15 points)	Y
4	CSA adder design 2 (no delay, 5 points)	Y
5	Four adder design with delay (10 points)	Y
6	Tradeoff between area and speed (Synthesis report, 10 points)	Y
7	Delay result/analysis (10 points)	Y
8	Any other discussion (10 points)	Y
9	Bonus: Submission date (+ ____ points)	

1. RCA adder design

```
module RCA(output [15:0] sum,output cout,input [15:0] ina,inb, input cin);  
  
    wire [4:1] c;  
    wire s1,s2;  
  
    fullAdder4 n1(sum[3:0],c[1],ina[3:0],inb[3:0],cin);  
    fullAdder4 n2(sum[7:4],c[2],ina[7:4],inb[7:4],c[1]);  
    fullAdder4 n3(sum[11:8],c[3],ina[11:8],inb[11:8],c[2]);  
    fullAdder4 n4(sum[15:12],cout,ina[15:12],inb[15:12],c[3]);  
  
endmodule
```

RCA

 

2. CLA adder design

```

module CLA(output [15:0] sum,
           output cout,
           input [15:0] ina,inb,
           input cin
           );


    wire [2:0] cout_t;

    CLA_4bit n1(sum[3:0],cout_t[0],ina[3:0],inb[3:0],cin);
    CLA_4bit n2(sum[7:4],cout_t[1],ina[7:4],inb[7:4],cout_t[0]);
    CLA_4bit n3(sum[11:8],cout_t[2],ina[11:8],inb[11:8],cout_t[1]);
    CLA_4bit n4(sum[15:12],cout,ina[15:12],inb[15:12],cout_t[2]);

endmodule

```

CLA

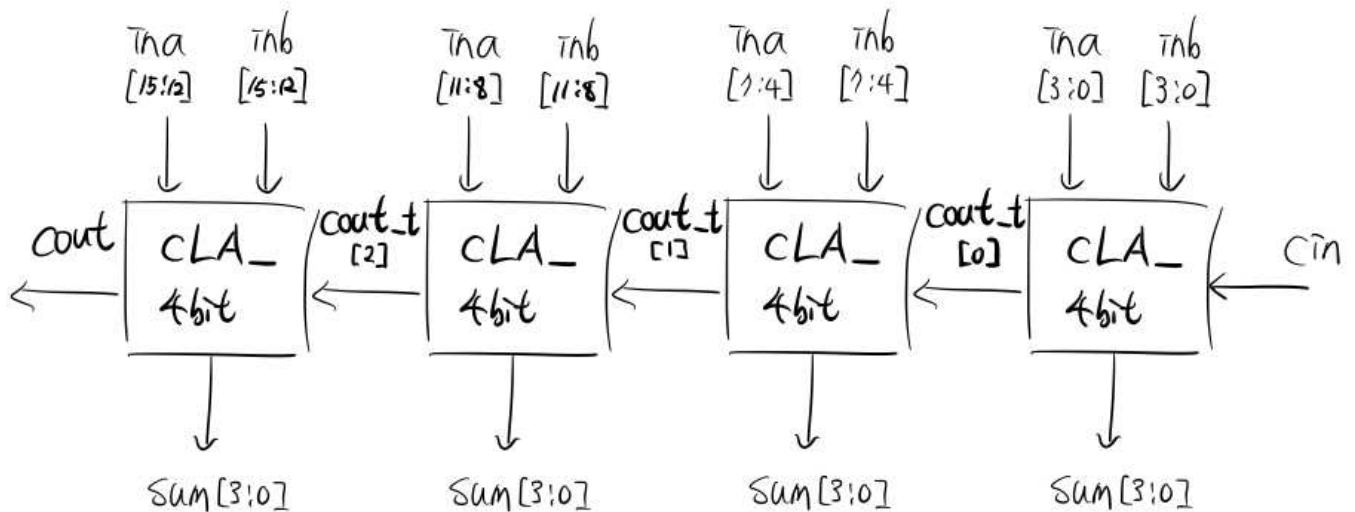

```

module CLA_4bit(
    output [3:0] sum,
    output cout,
    input [3:0] ina,inb,
    input cin
    );

    wire c1,c2,c3;
    wire [3:0] cout_t;

    CLB_4bit n1(c1,c2,c3,cout,ina,inb,cin);

```


```

fullAdder1 n2(sum[0],cout_t[0],ina[0],inb[0],cin);
fullAdder1 n3(sum[1],cout_t[1],ina[1],inb[1],c1);
fullAdder1 n4(sum[2],cout_t[2],ina[2],inb[2],c2);
fullAdder1 n5(sum[3],cout_t[3],ina[3],inb[3],c3);

```

endmodule

CLA_4bit

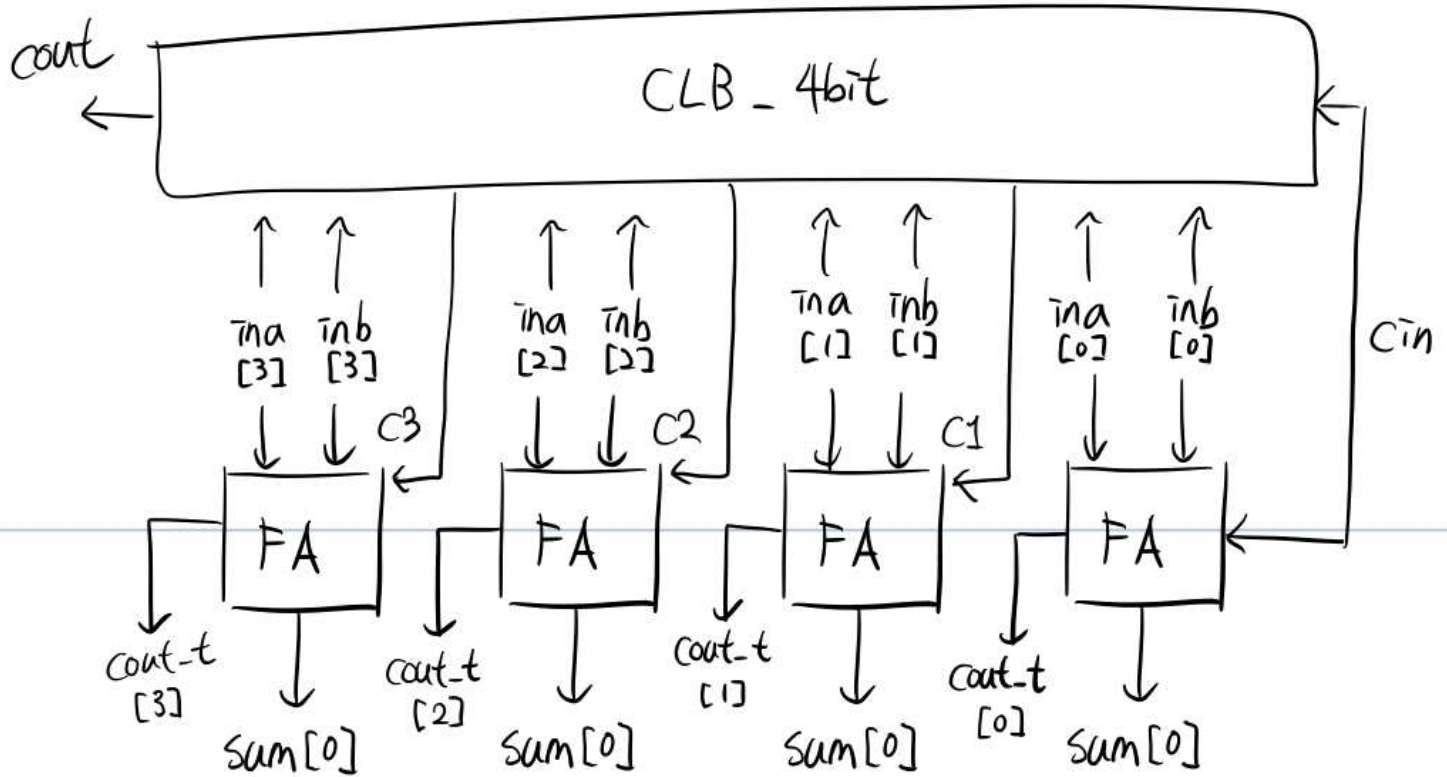

`timescale 1ns/1ns

module CLB_4bit(

output c1,c2,c3,cout,

input [3:0] ina,inb,

input cin

);

wire p0,p1,p2;

wire g0,g1,g2;

wire c1_t;

wire [3:0] c2_t;

wire [7:0] c3_t;

wire [12:0] c4_t;

```

// g0,p0
and n1(g0,ina[0],inb[0]);
xor n2(p0,ina[0],inb[0]);
// g1,p1
and n3(g1,ina[1],inb[1]);
xor n4(p1,ina[1],inb[1]);
// g2,p2
and n5(g2,ina[2],inb[2]);
xor n6(p2,ina[2],inb[2]);
// g3,p3
and n7(g3,ina[3],inb[3]);
xor n8(p3,ina[3],inb[3]);

//c1
and k1(c1_t,p0,cin);
or k2(c1,c1_t,g0);

//c2
and (c2_t[0],p1,p0,cin);
and (c2_t[1],p1,g0);

or (c2,g1,c2_t[1],c2_t[0]);

//c3
and (c3_t[0],p2,p1,p0,cin);
and (c3_t[1],p2,p1,g0);
and (c3_t[2],p2,g1);

or (c3,g2,c3_t[2],c3_t[1],c3_t[0]);

//cout
and (c4_t[0],p3,p2,p1,p0,cin);
and (c4_t[1],p3,p2,p1,g0);
and (c4_t[2],p3,p2,g1);
and (c4_t[3],p3,g2);

or (cout,g3,c4_t[3],c4_t[2],c4_t[1],c4_t[0]);
endmodule

```

CLB_4bit

$$\star G_i = \bar{a}[i] \cdot \bar{b}[i]$$

$$\star P_i = \bar{a}[i] \oplus \bar{b}[i]$$

$$\star C_1 = G_0 + P_0 \cdot C_{in}$$

$$\star C_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_{in}$$


$$\star C_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_{in}$$

$$\star C_{out} = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 \\ + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_{in}$$

3. CSA adder design 1

```
module CSA_1(output [15:0] sum, output cout, input [15:0] ina,inb, input cin);  
  
    wire [15:0] sum0;  
    wire cout_0;  
    wire [15:0] sum1;  
    wire cout_1;  
  
    reg cin_0;  
    reg cin_1;  
  
    CLA n1(sum0,cout_0,ina,inb,cin_0);  
    CLA n2(sum1,cout_1,ina,inb,cin_1);  
  
    MUX21 a0(cout,cout_0,cout_1,cin);  
  
    MUX21 a1(sum,sum0,sum1,cin);  
  
    initial begin  
        cin_0 = 0;  
        cin_1 = 1;  
    end  
  
endmodule
```

CSA-1

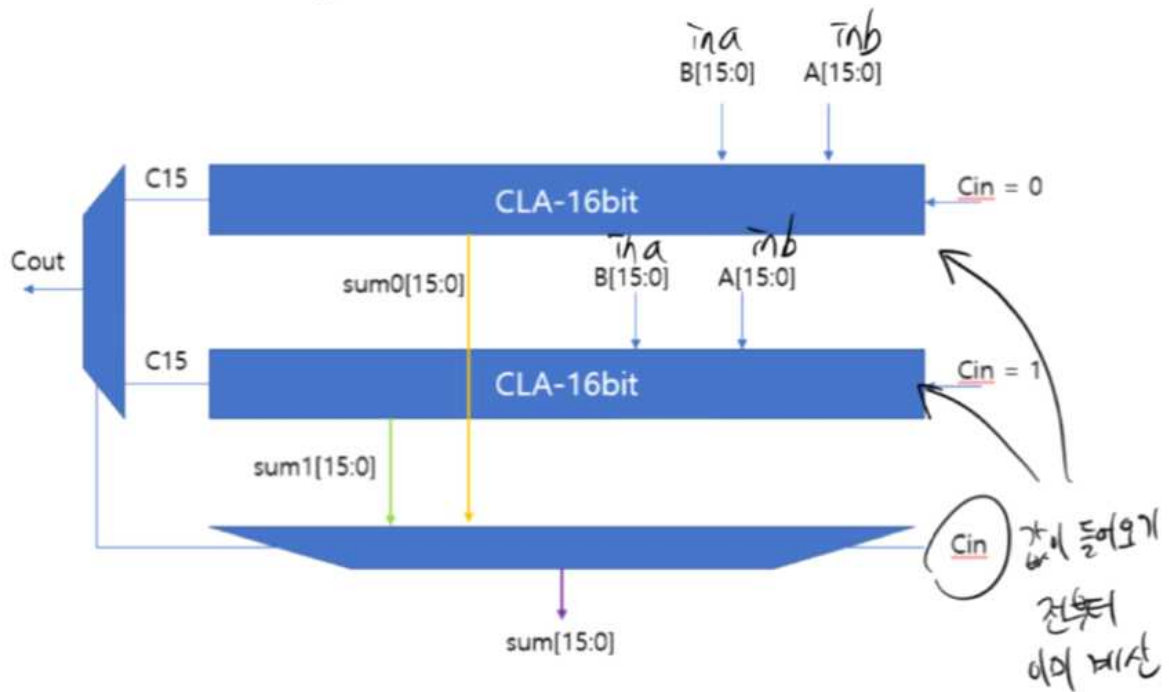

4. CSA adder design 2

```
module CSA_2(output [15:0] sum, output cout, input [15:0] ina,inb, input cin);
```

```
    wire [15:0] sum0;
    wire cout_0;
    wire [15:0] sum1;
    wire cout_1;
```

```
    reg cin_0;
    reg cin_1;
```

```
    RCA n1(sum0,cout_0,ina,inb,cin_0);
    RCA n2(sum1,cout_1,ina,inb,cin_1);
```

```
    MUX21 a0(cout,cout_0,cout_1,cin);
```

```
    MUX21 a1(sum,sum0,sum1,cin);
```


```
    initial begin
        cin_0 = 0;
```

cin_1 = 1;

end

endmodule

CSA-2

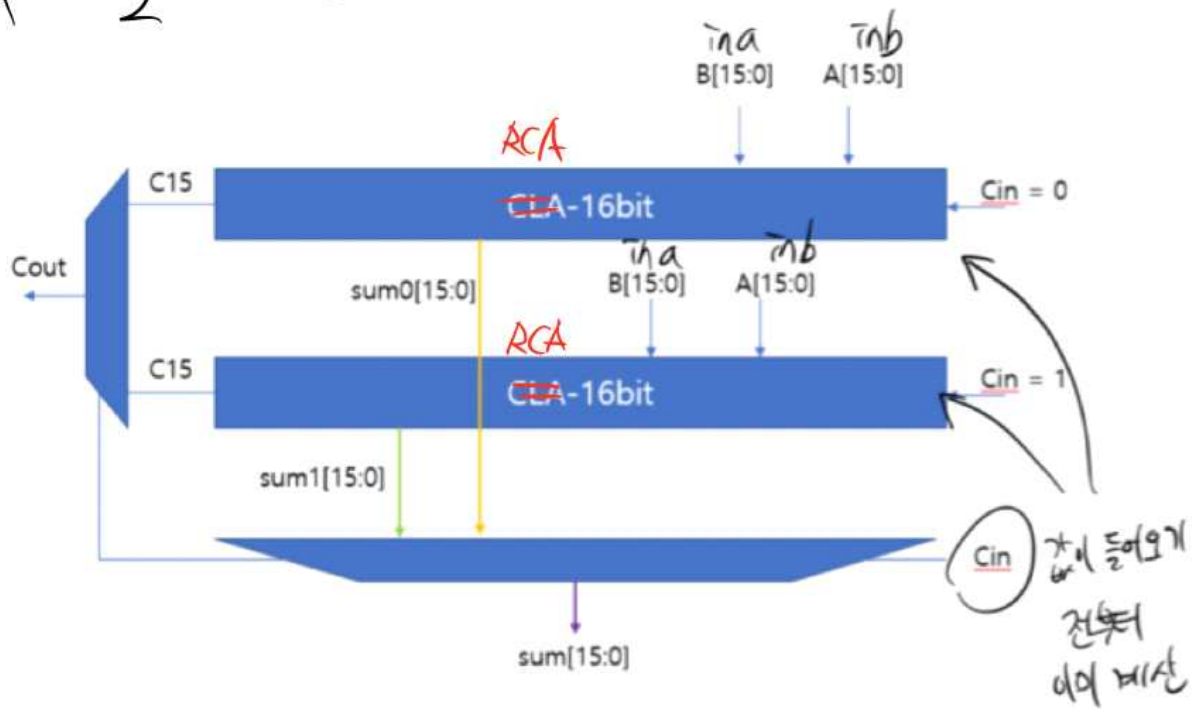

5. Four adder design with delay

1. RCA with delay

we need to change only “fullAdder1” module.

```
`timescale 1ns/1ns
module fullAdder1(output sum,c_out, input a,b,c_in);
    wire s1,c1,s2;

    xor #(6) n1(s1,a,b);
    and #(7) n2(c1,a,b);
    xor #(6) n3(sum,s1,c_in);
    and #(7) n4(s2,s1,c_in);
    xor #(6) n5(c_out,s2,c1);

endmodule
```

2. CLA with delay

we need to change only “CLB_4bit” module.

```
`timescale 1ns/1ns
module CLB_4bit(
    output c1,c2,c3,cout,
    input [3:0] ina,inb,
    input cin
);

    wire p0,p1,p2;
    wire g0,g1,g2;

    wire c1_t;
    wire [3:0] c2_t;
    wire [7:0] c3_t;
    wire [12:0] c4_t;

    // g0,p0
    and #(7) n1(g0,ina[0],inb[0]);
    xor #(6) n2(p0,ina[0],inb[0]);
    // g1,p1
    and #(7) n3(g1,ina[1],inb[1]);
    xor #(6) n4(p1,ina[1],inb[1]);
    // g2,p2
    and #(7) n5(g2,ina[2],inb[2]);
    xor #(6) n6(p2,ina[2],inb[2]);
```

```

// g3,p3
and #(7) n7(g3,ina[3],inb[3]);
xor #(6) n8(p3,ina[3],inb[3]);

//c1
and #(7) k1(c1_t,p0,cin);
or #(7) k2(c1,c1_t,g0);

//c2
and #(7) (c2_t[0],p1,p0,cin);
and #(7) (c2_t[1],p1,g0);

or #(7) (c2,g1,c2_t[1],c2_t[0]);

//c3
and #(7) (c3_t[0],p2,p1,p0,cin);
and #(7) (c3_t[1],p2,p1,g0);
and #(7) (c3_t[2],p2,g1);

or #(7) (c3,g2,c3_t[2],c3_t[1],c3_t[0]);

//cout
and #(7) (c4_t[0],p3,p2,p1,p0,cin);
and #(7) (c4_t[1],p3,p2,p1,g0);
and #(7) (c4_t[2],p3,p2,g1);
and #(7) (c4_t[3],p3,g2);

or #(7) (cout,g3,c4_t[3],c4_t[2],c4_t[1],c4_t[0]);

```

endmodule

3. CSA_1 with delay

Just add MUX delay to CSA_1 module

```

module CSA_1(output [15:0] sum, output cout, input [15:0] ina,inb, input cin);

```

```

    wire [15:0] sum0;
    wire cout_0;
    wire [15:0] sum1;
    wire cout_1;

```

```

    reg cin_0;
    reg cin_1;

```

```

    CLA n1(sum0,cout_0,ina,inb,cin_0);

```

```
CLA n2(sum1,cout_1,ina,inb,cin_1);
```

```
MUX21 #(3) a0(cout,cout_0,cout_1,cin);
```

```
MUX21 #(3) a1(sum,sum0,sum1,cin);
```

```
initial begin  
    cin_0 = 0;  
    cin_1 = 1;  
end
```

```
endmodule
```

4. CSA_2 with delay

Just add MUX delay to CSA_2 module

```
module CSA_2(output [15:0] sum, output cout, input [15:0] ina,inb, input cin);
```

```
wire [15:0] sum0;  
wire cout_0;  
wire [15:0] sum1;  
wire cout_1;
```

```
reg cin_0;  
reg cin_1;
```

```
RCA n1(sum0,cout_0,ina,inb,cin_0);  
RCA n2(sum1,cout_1,ina,inb,cin_1);
```

```
MUX21 #(3) a0(cout,cout_0,cout_1,cin);
```

```
MUX21 #(3) a1(sum,sum0,sum1,cin);
```

```
initial begin  
    cin_0 = 0;  
    cin_1 = 1;  
end
```

```
endmodule
```

=> reference

MUX design

```
`timescale 1ns/1ns
module MUX21 #(parameter delay=0) (output reg [15:0] sum,input [15:0] in0, in1, input sel);

    always @(*) begin
        #delay
        case (sel)
            1'b0:sum = in0;
            1'b1:sum = in1;
        endcase
    end
end

endmodule
```

6. Tradeoff between area and speed

----- how fast

1. RCA

XOR => 48 units

AND => 32 units

80 unit ----- slowest (4)

2. CLA

AND => 88 units

XOR => 64 units

OR => 16 units

168 units ----- fast (2)

3. CSA_1

AND => 176 units

XOR => 128 units

OR => 32 units

336 units ----- fastest (1)

4. CSA_2

XOR => 96 units

AND => 64 units

160 units ----- slow (3)

we can know tradeoff between area and speed

by correlation between above gate unit calculation and speed




The more gates the adder has, the better the performance of the adder.

7. Delay result/analysis

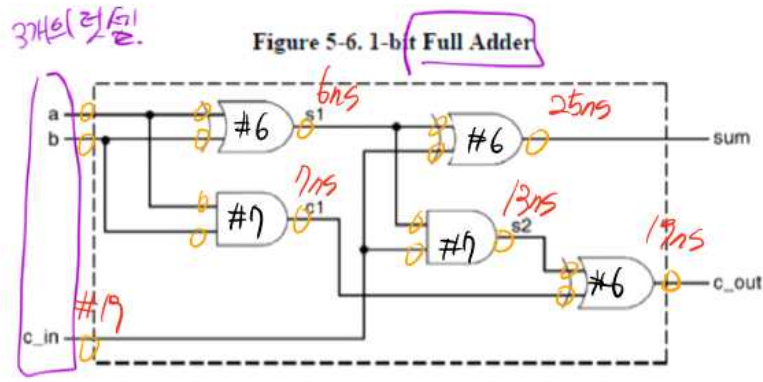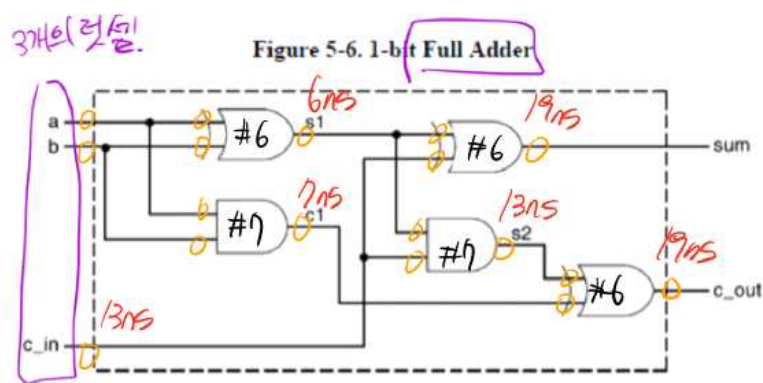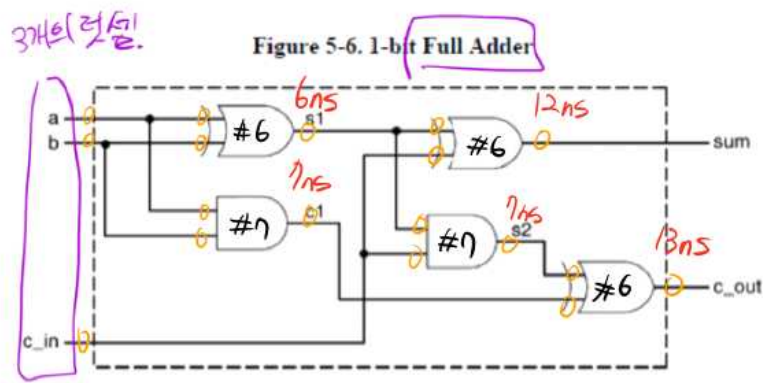
1)



The reason why the RCA is fastest module is that the result of AND gates can be decided by just one input.



2)

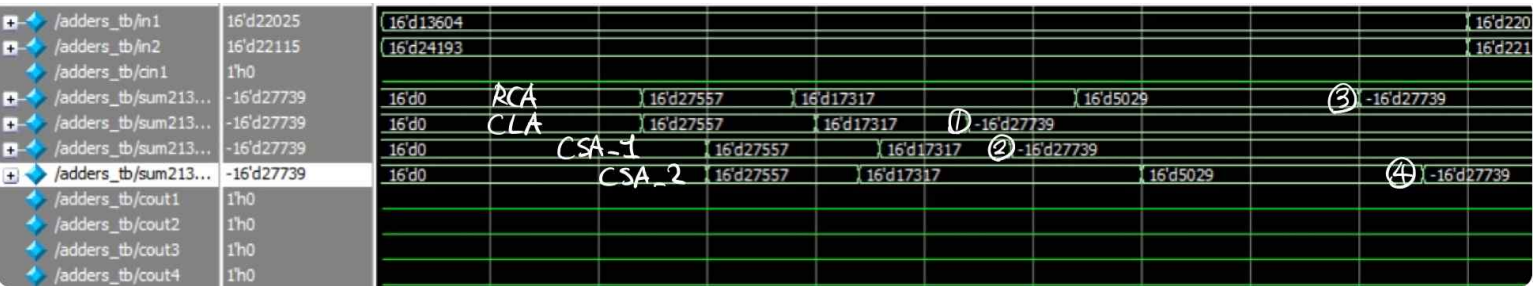

this part is the result that we expect.

fastest => CLA

fast => CSA_1


slow => RCA

slowest => CSA_2

At this time, speed of CSA is slower than CLA or RCA.

but CSA is much better than CLA or RCA when the cin1 changes suddenly.


3)

 

The more difficult the AND gate is to predict the result,

the larger the performance difference between CLA and RCA.

4)

 

CSA1 and CSA2 show tremendous performance when the value of cin1 suddenly changes because they calculate the value in advance.

8. Any other discussion

1. The reason Why RCA is the slowest adder

=> Since RCA always has to do the calculations in order, you have to wait until the adder in the previous order completes the calculation.

2. The reason Why CLA is faster than RCA

=> Because we calculate all carry at once and add all at once.

3. The reason why we use CSA

=> CSA calculates all situations of cin input in advance, which is very useful when the cin input suddenly changes.

4. The reason why CSA-2 is slower than CSA-1

=> CSA-2 uses RCA by default, so it's slower than CSA-1 using CLA.

5. When one input of an AND gate inside the RSA is zero, the performance of the RSA is greatly improved.

This is because the delay is applied if the result can be specified regardless of the change in the input.